

Indian Institute of Technology Bombay



IITB CPU
Project Report

by

TEAM ID: 11

Takshit Aggarwal (22B1236)

Harsh Anand (22B1249)

Medhansh Sharma (22B1287)

Sarthak Niranjana (22B3923)

Course Instructor


Prof. Virendra Singh,
Department of Electrical Engineering,
IIT Bombay.

EE 224 : Digital Systems
Course Project
Autumn, 2023

Objective

This project required us to develop a 16-bit computing system named IITB-CPU with a specified instruction set architecture. We were required to implement the system using VHDL as the Hardware Description Language (HDL). The IITB-CPU should features an 8-register architecture and operate on 16-bit data, utilizing a point-to-point communication infrastructure for efficient data exchange.

Simulation

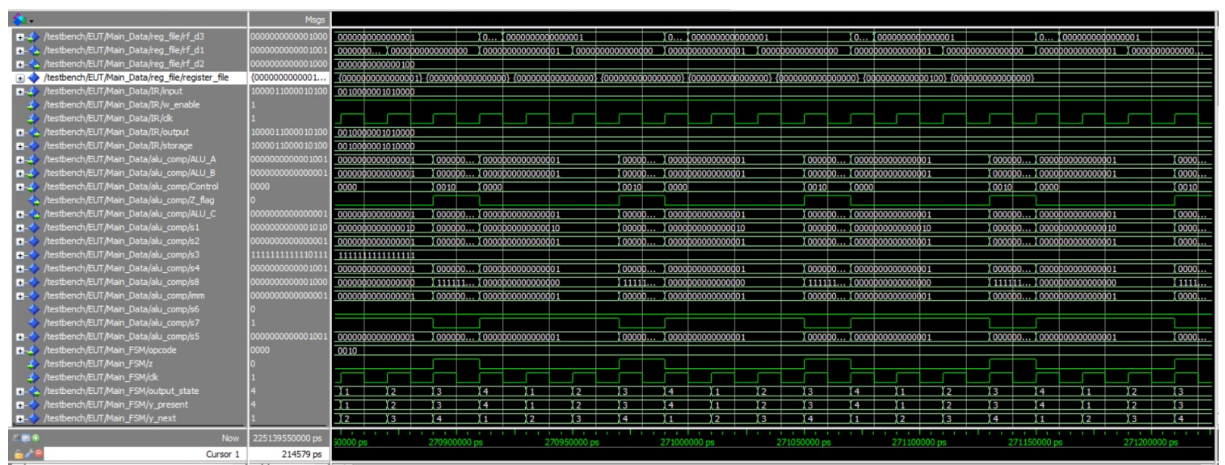

All States

§1

- RF_A1 -> 111
- Mem_Add -> RF_D1
- IR_in -> Memory
- OpCode -> IR_out(15:12)

§3

- OpCode -> IR(15:12)
- ALU_A -> T1_out
- ALU_B -> T2_out
- T3_in -> ALU_C

§5

- RF_A1 -> IR_out(11:9)
- T1_in -> RF_D1
- SE10_in -> IR_out(5:0)
- T2 -> SE10
- RF_A3 -> IR_out(8:6)

§7

- SE7_in -> IR_out(8:0)
- L8_in -> SE7_out
- T1_in -> L8_out
- RF_A3 -> IR_out(11:9)
- RF_D3 -> T1_out

§9

- RF_A1 -> "111"
- ALU_A -> T1_out
- ALU_B -> T2_out
- ALU_A -> RF_D1
- SE10_in -> IR_out (5:0)
- ALU_b -> SE_10_out
- RF_A3 -> "111"
- RF_D3 -> ALU_C

§2

- RF_A1 -> IR_out(11:0)
- RF_A2 -> IR_out(8:6)
- T1_in -> RF_D1
- T2_in -> RF_D2
- RF_A3 -> IR_out(5:3)

§4

- RF_A1 -> 111
- ALU_A -> RF_D1
- ALU_B -> 0000000000000001
- RF_A3 -> 111
- RF_D3 -> ALU_C

§6

- SE7_in -> IR_out(8:0)
- T1_in -> SE7_out
- RF_A3 -> IR_out(11:9)
- RF_D3 -> T1_out

§8

- RF_A1 -> IR_out(11:9)
- RF_A2 -> IR_out(8:6)
- T1_in -> RF_D1
- T2_in -> RF_D2

§10

- RF_A1 -> "111"
- ALU_A -> T1_out
- ALU_B -> T2_out
- ALU_A -> RF_D1
- ALU_b -> "0000000000000001"
- RF_A3 -> "111"
- RF_D3 -> ALU_C

S11

- RF_A1 -> "111"
- RF_A3 -> IR_OUT (11:9)
- RF_D3 -> RF_D1
- T1_in -> Rf_D1
- SE10_in -> IR_out (5:0)
- T2_in -> SE10_out

S12

- ALU_C -> T1_out
- ALU_B -> T2_out
- RF_A3 -> "111"
- Rf_D3 -> ALU_C

S14

- RF_A1 -> IR_out (8:6)
- RFRf_A3 -> "111"
- RF_D3 -> RF_D1

S15

- RF_A2 -> IR_out(8:6)
- ALU_B -> RF_D2
- SE10_in -> IR_out(5:0)
- ALU_A -> SE10_out
- M_A -> ALU_C

S17

- RF_A1 -> IR_out (11:9)
- T1_in -> RF_D1
- M_in -> T1_out

S13

- RF_A1 -> "111"
- RF_A3 -> IR_out(11:9)
- RF_D3 -> Rf_D1

S16


- RF_A3 -> IR_out (11:9)
- RF_D3 -> M_out

Instruction State Diagrams


ADD / SUB / MUL / AND / ORA / IMP



ADI

 

LHI / LLI

 

BEO






JAL



JLR





LW

 

SW



 

 

Contributions

Takshit Aggarwal (Project Leader) :

- Handled distribution and supervision of work among team members.
- Encoded the multiplexers used for controlling the Datapath in VHDL.
- Wrote the VHDL code for a hard-coded Memory.
- Helped in designing and coding the Datapath and Control signals for the system.
- Helped in Debugging the code to ensure proper functioning.

Harsh Anand :

- Designed the pen-paper State Machine Diagrams of the instructions.
- Encoded the registers used to store data in VHDL.
- Helped in encoding the state machines in VHDL.
- Contributed to compiling our progress in a detailed Project Report.

Medhansh Sharma :

- Encoded the components such as sign extender, register file and left shifters.
- Helped in designing and coding the Datapath and Control signals for the system.
- Wrote the VHDL code for ALU used for performing multiple different operations as required.
- Helped in Debugging the code to ensure proper functioning.

Sarthak Niranjana :

- Helped in designing and encoding the state machines in VHDL.
- Wrote the VHDL code for CPU used for integrating the Datapath with the State Machine encoded previously.
- Contributed to compiling our progress in a detailed Project Report.

Changes

January 30, 2024

- A 6x1 mux was added to the ALU to synchronise it with the clock of CPU
- ALU was coded in behavioral modelling earlier but as structural modelling gave better result so we changed the ALU to structural modelling
- A functional reset button was added to the CPU
- The LEDs were mapped to various registers and memory and the switches were used to alternate between them
- Some of the instructions whoser simulations were not working earlier were improved by adding extra states which made the other functions functional.
- A functional reset button was added to the CPU